 


LIST OF EXPERIMENTS


1. Verification of Logic Gates and Boolean theorems.
2. Design and implementation of adder and subtractor
3. Design and implementation of Encoder and Decoder.
4. Design and implementation of Multiplexer and Demultiplexer.
5. Design and implementation of Parity generator/checker.
6. Design and implementation of Shift registers
7. Simple 8085 Assembly Language Programs: 8 bit Arithmetic operations
8. Interfacing and Programming of 8255- Programmable Peripheral Interface
9. Interfacing of a stepper motor with 8085 microprocessor
10. Interfacing of a traffic light controller with 8085 microprocessor

2-Input AND gate:**LOGIC DIAGRAM****TRUTH TABLE**

| INPUTS | | OUTPUT |
|--------|---|--------|
| a | b | c |
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

OUTPUT TABLE


| INPUTS | | OUTPUT |
|--------|---|--------|
| a | b | c |
| 0 | 0 | |
| 0 | 1 | |
| 1 | 0 | |
| 1 | 1 | |

 2-Input OR gate:**LOGIC DIAGRAM****TRUTH TABLE**

| INPUTS | | OUTPUT |
|--------|---|--------|
| a | b | c |
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

OUTPUT TABLE


| INPUTS | | OUTPUT |
|--------|---|--------|
| a | b | c |
| 0 | 0 | |
| 0 | 1 | |
| 1 | 1 | |
| 1 | 1 | |

 NOT gate:**LOGIC DIAGRAM****TRUTH TABLE**

| INPUTS | OUTPUT |
|----------|----------|
| a | c |
| 0 | 1 |
| 1 | 0 |

OUTPUT TABLE

| INPUTS | OUTPUT |
|--------|--------|
| a | c |
| 0 | |
| 1 | |

 2- Input NAND gate:**LOGIC DIAGRAM****TRUTH TABLE**

| INPUTS | | OUTPUT |
|--------|---|--------|
| a | b | c |
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

OUTPUT TABLE

| INPUTS | | OUTPUT |
|--------|---|--------|
| a | b | c |
| 0 | 0 | |
| 0 | 1 | |
| 1 | 0 | |
| 1 | 1 | |

Expt. No.: 1

Date:

VERIFICATION OF LOGIC GATES AND BOOLEAN THEOREMS**Aim**


To verify the truth table of AND gate, OR gate, NOT gate, NAND gate, NOR gate, Exclusive-OR gate and Exclusive-NOR gate and Boolean theorems.

Components Required

| S. No. | Description | Specification | Quantity |
|--------|-------------------------|---------------|-------------|
| 1. | 2-input AND Gate | IC 7408/4081 | 1 |
| 2. | 2-input OR Gate | IC 7432/4071 | 1 |
| 3. | Hex Inverter (NOT Gate) | IC 7404/4069 | 1 |
| 4. | 2-input NAND Gate | IC 7400/4011 | 1 |
| 5. | 2-input NOR Gate | IC 7402/4001 | 1 |
| 6. | 2-input X-OR Gate | IC 7486/4030 | 1 |
| 7. | Digital Trainer Kit | - | 1 |
| 8. | Bread board | - | 1 |
| 9. | Power Supply | 5V | 1 |
| 10. | Connecting wires | - | As Required |

Procedure:


- Make the connections as per the logic diagram.
- Switch on the power supply.
- Apply various combinations of inputs using the switches according to the truth table and observe the condition of output LEDs.
- Note down the output as '1' when the LED is 'ON' and as '0' when the LED is 'OFF'.

 2- Input NOR gate:**LOGIC DIAGRAM****TRUTH TABLE**

| INPUTS | | OUTPUT |
|--------|---|--------|
| a | b | c |
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

OUTPUT TABLE


| INPUTS | | OUTPUT |
|--------|---|--------|
| a | b | c |
| 0 | 0 | |
| 0 | 1 | |
| 1 | 0 | |
| 1 | 1 | |

 2- Input XOR gate:**LOGIC DIAGRAM****TRUTH TABLE**

| INPUTS | | OUTPUT |
|--------|---|--------|
| a | b | c |
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

OUTPUT TABLE

| INPUTS | | OUTPUT |
|--------|---|--------|
| a | b | c |
| 0 | 0 | |
| 0 | 1 | |
| 1 | 0 | |
| 1 | 1 | |

 2- Input XNOR gate:**LOGIC DIAGRAM****TRUTH TABLE**


| INPUTS | | OUTPUT |
|--------|---|--------|
| a | b | c |
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

OUTPUT TABLE

| INPUTS | | OUTPUT |
|--------|---|--------|
| a | b | c |
| 0 | 0 | |
| 0 | 1 | |
| 1 | 0 | |
| 1 | 1 | |

Distributive Theorem:

$$A + (B.C) = (A + B) . (A + C)$$

 **Output Table:**

| INPUTS | | | OUTPUTS | | | | |
|--------|---|---|---------|-----------|-------|-------|-----------------|
| A | B | C | B.C | A + (B.C) | A + B | A + C | (A + B).(A + C) |
| 0 | 0 | 0 | | | | | |
| 0 | 0 | 1 | | | | | |
| 0 | 1 | 0 | | | | | |
| 0 | 1 | 1 | | | | | |
| 1 | 0 | 0 | | | | | |
| 1 | 0 | 1 | | | | | |
| 1 | 1 | 0 | | | | | |
| 1 | 1 | 1 | | | | | |

Result

| | | |
|--------------------|-----|--|
| PREPARATION | 30 | |
| LAB PERFORMANCE | 30 | |
| REPORT | 40 | |
| TOTAL | 100 | |
| INITIAL OF FACULTY | | |

HALF ADDER:**Truth Table:**

| INPUTS | | OUTPUTS | |
|--------|---|---------|-----|
| X | Y | Carry | Sum |
| 0 | 0 | | |
| 0 | 1 | | |
| 1 | 0 | | |
| 1 | 1 | | |

K-Map for Carry:

| | | |
|-------|---|---|
| X \ Y | 0 | 1 |
| 0 | | |
| 1 | | |

Carry =

K-Map for Sum:

| | | |
|-------|---|---|
| X \ Y | 0 | 1 |
| 0 | | |
| 1 | | |

Sum =

Logic diagram:**Output Table:**

| INPUTS | | OUTPUTS | |
|--------|---|---------|-----|
| X | Y | Carry | Sum |
| 0 | 0 | | |
| 0 | 1 | | |
| 1 | 0 | | |
| 1 | 1 | | |

HALF SUBTRACTOR:**Truth Table:**

| INPUTS | | OUTPUTS | |
|--------|---|---------|------------|
| X | Y | Borrow | Difference |
| 0 | 0 | | |
| 0 | 1 | | |
| 1 | 0 | | |
| 1 | 1 | | |

Expt. No.: 2

DESIGN AND IMPLEMENTATION OF ADDER AND SUBTRACTOR

Date:

Aim:

To design and implement Half adder / subtractor and Full adder/subtractor using Digital logic gates.

Components Required:

| S. No. | Description | Specification | Quantity |
|--------|---------------------|---------------|-------------|
| 1. | 2-input AND Gate | IC 4081/7408 | 1 |
| 2. | 2-input OR Gate | IC 4071/7432 | 1 |
| 3. | NOT Gate | IC 4069/7404 | 1 |
| 4. | 2-input XOR Gate | IC 4030/7486 | 1 |
| 5. | Digital Trainer Kit | - | 1 |
| 6. | Bread board | - | 1 |
| 7. | Power Supply | 5V | 1 |
| 8. | Connecting wires | - | As Required |

Procedure:

- (i) Create the truth table according to the logic of the adder/subtractor.
- (ii) Derive the expression for the output using k-map.
- (iii) Draw the logic diagram.
- (iv) Make the connections as per the logic diagram.
- (v) Switch on the power supply.
- (vi) Apply various combinations of inputs according to the truth table and observe the conditions of the output LEDs.
- (vii) Note down the output for half adder/full adder (sum, carry) and half subtractor/full (difference, borrow) for different combinations of inputs.

K-Map for Borrow:

| X \ Y | 0 | 1 |
|-------|---|---|
| | | |
| 0 | | |
| 1 | | |

Borrow =**K-Map for Difference:**

| X \ Y | 0 | 1 |
|-------|---|---|
| | | |
| 0 | | |
| 1 | | |

Difference =**Logic diagram:****Output Table:**

| INPUTS | | OUTPUTS | |
|--------|---|---------|------------|
| X | Y | Borrow | Difference |
| 0 | 0 | | |
| 0 | 1 | | |
| 1 | 0 | | |
| 1 | 1 | | |

FULL ADDER:**Truth Table:**

| INPUTS | | | OUTPUTS | |
|--------|---|---|---------|-----|
| X | Y | Z | Carry | Sum |
| 0 | 0 | 0 | | |
| 0 | 0 | 1 | | |
| 0 | 1 | 0 | | |
| 0 | 1 | 1 | | |
| 1 | 0 | 0 | | |
| 1 | 0 | 1 | | |
| 1 | 1 | 0 | | |
| 1 | 1 | 1 | | |

K-Map for Carry:

| X \ Y Z | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| | | | | |
| 0 | | | | |
| 1 | | | | |

Carry =

K-Map for Sum:

| X \ Y Z | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| | | | | |
| 0 | | | | |
| 1 | | | | |

Sum =

Logic diagram:**Output Table:**

| INPUTS | | | OUTPUTS | |
|--------|---|---|---------|-----|
| X | Y | Z | Carry | Sum |
| 0 | 0 | 0 | | |
| 0 | 0 | 1 | | |
| 0 | 1 | 0 | | |
| 0 | 1 | 1 | | |
| 1 | 0 | 0 | | |
| 1 | 0 | 1 | | |
| 1 | 1 | 0 | | |
| 1 | 1 | 1 | | |

FULL SUBTRACTOR:**Truth Table:**

| INPUTS | | | OUTPUTS | |
|--------|---|---|---------|------------|
| X | Y | Z | Borrow | Difference |
| 0 | 0 | 0 | | |
| 0 | 0 | 1 | | |
| 0 | 1 | 0 | | |
| 0 | 1 | 1 | | |
| 1 | 0 | 0 | | |
| 1 | 0 | 1 | | |
| 1 | 1 | 0 | | |
| 1 | 1 | 1 | | |

K-Map for Borrow:

| X \ Y Z | | | | |
|---------|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 0 | | | | |
| 1 | | | | |

Borrow =**K-Map for Difference:**


| X \ Y Z | | | | |
|---------|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 0 | | | | |
| 1 | | | | |

Difference =**Logic diagram:****Output Table:**

| INPUTS | | | OUTPUTS | |
|--------|---|---|---------|------------|
| X | Y | Z | Borrow | Difference |
| 0 | 0 | 0 | | |
| 0 | 0 | 1 | | |
| 0 | 1 | 0 | | |
| 0 | 1 | 1 | | |
| 1 | 0 | 0 | | |
| 1 | 0 | 1 | | |
| 1 | 1 | 0 | | |
| 1 | 1 | 1 | | |

Result:


| | | |
|---------------------------|------------|--|
| PREPARATION | 30 | |
| LAB PERFORMANCE | 30 | |
| REPORT | 40 | |
| TOTAL | 100 | |
| INITIAL OF FACULTY | | |

 4:1 MULTIPLEXER:**Pin Diagram:****Truth Table:**

| SELECT LINES | | OUTPUT |
|--------------|---|--------|
| B | A | Y |
| 0 | 0 | D0 |
| 0 | 1 | D1 |
| 1 | 0 | D2 |
| 1 | 1 | D3 |

$$Y = B'.A'.D0 + B'.A.D1 + B.A'.D2 + B.A.D3$$

DATA INPUTS : D0, D1, D2, D3

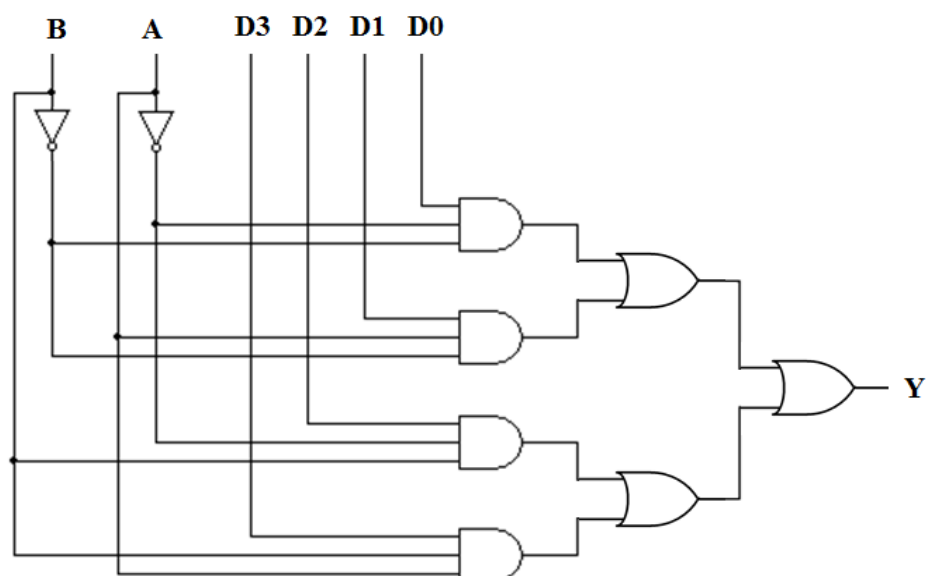Internal Connection of IC 4051:

Expt. No.: 3**Date:****DESIGN AND IMPLEMENTATION OF MULTIPLEXER AND DEMULTIPLEXER****Aim:**

To design and implement Multiplexer and Demultiplexer using Digital IC 4051 and IC 4555 respectively.

Components Required:


| S. No. | Description | Specification | Quantity |
|--------|-----------------------|---------------|-------------|
| 1. | Multiplexer | IC 4051 | 1 |
| 2. | Decoder/Demultiplexer | IC 4555/4556 | 1 |
| 3. | Digital Trainer Kit | - | 1 |
| 4. | Bread board | - | 1 |
| 5. | Power Supply | 5V | 1 |
| 6. | Connecting wires | - | As Required |

Procedure:

- (i) Make the connections as per the logic diagram.
- (ii) Switch on the power supply.
- (iii) Apply various combinations of inputs according to the truth table and observe condition of output LEDs.
- (iv) Note down the outputs of multiplexer and Demultiplexer for different combinations of input.

Output Table:

| SELECT LINES | | INPUTS | | | | OUTPUT |
|--------------|---|--------|----|----|----|--------|
| B | A | D3 | D2 | D1 | D0 | Y |
| 0 | 0 | 0 | 0 | 0 | 0 | |
| | | 0 | 1 | 1 | 1 | |
| 0 | 1 | 1 | 0 | 0 | 0 | |
| | | 0 | 1 | 1 | 0 | |
| 1 | 0 | 0 | 0 | 1 | 0 | |
| | | 0 | 1 | 0 | 0 | |
| 1 | 1 | 1 | 0 | 0 | 0 | |
| | | 0 | 1 | 0 | 1 | |

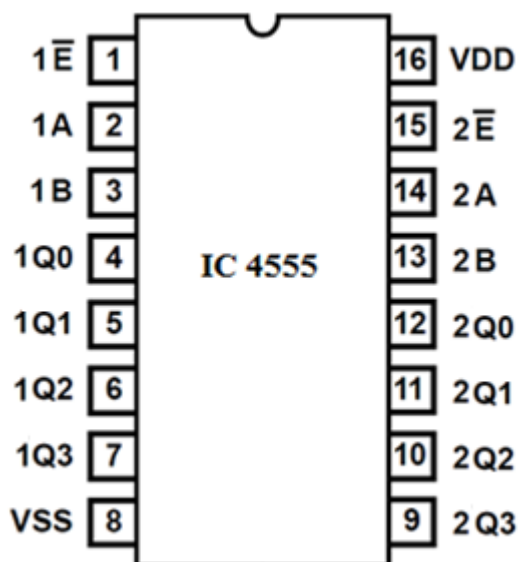1:4 DEMULTIPLEXER:**Pin Diagram:**

Note: The Data input D must be inverted and given at either $\overline{1E}$ or $\overline{2E}$

Truth Table:

| DATA INPUT | SELECT LINES | | OUTPUTS | | | |
|------------|--------------|---|---------|----|----|----|
| | B | A | Q3 | Q2 | Q1 | Q0 |
| D | 0 | 0 | 0 | 0 | 0 | D |
| D | 0 | 1 | 0 | 0 | D | 0 |
| D | 1 | 0 | 0 | D | 0 | 0 |
| D | 1 | 1 | D | 0 | 0 | 0 |


$$Q0 = D \cdot B' \cdot A'$$

$$Q1 = D \cdot B' \cdot A$$

$$Q2 = D \cdot B \cdot A'$$

$$Q3 = D \cdot B \cdot A$$

Internal Connection of IC 4555:

 


Output Table:

| SELECT LINES | | INPUT | OUTPUTS | | | |
|--------------|---|-------|---------|----|----|----|
| B | A | D | Q3 | Q2 | Q1 | Q0 |
| 0 | 0 | 0 | | | | |
| | | 1 | | | | |
| 0 | 1 | 0 | | | | |
| | | 1 | | | | |
| 1 | 0 | 0 | | | | |
| | | 1 | | | | |
| 1 | 1 | 0 | | | | |
| | | 1 | | | | |

Result:

| | | |
|--------------------|-----|--|
| PREPARATION | 30 | |
| LAB PERFORMANCE | 30 | |
| REPORT | 40 | |
| TOTAL | 100 | |
| INITIAL OF FACULTY | | |

 
8-TO-3 LINE ENCODER:**Pin Diagram:****Truth Table:**

| INPUTS | | | | | | | | OUTPUTS | | |
|--------|----|----|----|----|----|----|----|---------|----|----|
| D7 | D6 | D5 | D4 | D3 | D2 | D1 | D0 | Q2 | Q1 | Q0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 |

$$Q2 = D4 + D5 + D6 + D7$$

$$Q1 = D2 + D3 + D6 + D7$$

$$Q0 = D1 + D3 + D5 + D7$$

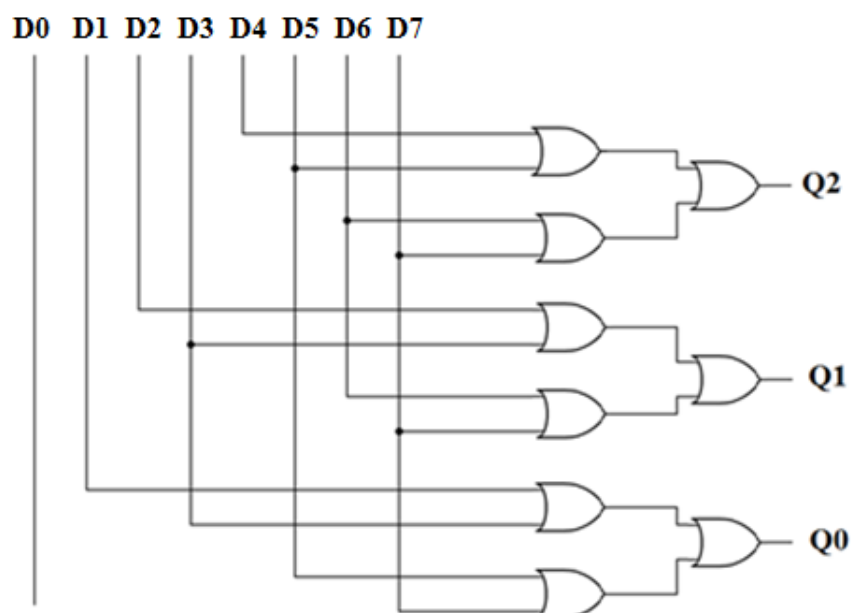Internal Connection of IC 4532:

Expt. No.: 4**Date:****DESIGN AND IMPLEMENTATION OF ENCODER AND DECODER****Aim**

To design and implement Encoder and Decoder using Digital IC 4532 and IC 4555 respectively.

Components Required


| S. No. | Description | Specification | Quantity |
|--------|-----------------------|---------------|-------------|
| 1. | Encoder | IC 4532 | 1 |
| 2. | Decoder/Demultiplexer | IC 4555/4556 | 1 |
| 3. | Digital Trainer Kit | - | 1 |
| 4. | Bread board | - | 1 |
| 5. | Power Supply | 5V | 1 |
| 6. | Connecting wires | - | As Required |

Procedure

- (i) Make the connections as per the logic diagram.
- (ii) Switch on the power supply.
- (iii) Apply various combinations of inputs according to the truth table and observe condition of output LEDs.
- (iv) Note down the outputs of encoder and decoder for different combinations of input.

Output Table:

| INPUTS | | | | | | | | | OUTPUTS | | | | |
|--------|----|----|----|----|----|----|----|----|---------|----|----|----|----|
| EI | D7 | D6 | D5 | D4 | D3 | D2 | D1 | D0 | Q2 | Q1 | Q0 | GS | E0 |
| 0 | X | X | X | X | X | X | X | X | | | | | |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | | | | | |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | | | | | |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | | | | | |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | | | | | |
| 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | | | | | |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | | | | | |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | | | | | |
| 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | | | | | |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | | | | | |

 3-TO-8 LINE DECODER:**Pin Diagram:****Truth Table:**

| INPUTS | | | OUTPUTS | | | | | | | |
|--------|---|---|---------|----|----|----|----|----|----|----|
| C | B | A | Q7 | Q6 | Q5 | Q4 | Q3 | Q2 | Q1 | Q0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |

$$Q0 = C'.B'.A'$$

$$Q1 = C'.B'.A$$

$$Q2 = C'.B.A'$$

$$Q3 = C'.B.A$$


$$Q4 = C.B'.A'$$

$$Q5 = C.B'.A$$

$$Q6 = C.B.A'$$

$$Q7 = C.B.A$$

Internal Connection of IC 4555:

 


Output Table:

| INPUTS | | | OUTPUTS | | | | | | | |
|--------|---|---|---------|----|----|----|----|----|----|----|
| C | B | A | Q7 | Q6 | Q5 | Q4 | Q3 | Q2 | Q1 | Q0 |
| 0 | 0 | 0 | | | | | | | | |
| 0 | 0 | 1 | | | | | | | | |
| 0 | 1 | 0 | | | | | | | | |
| 0 | 1 | 1 | | | | | | | | |
| 1 | 0 | 0 | | | | | | | | |
| 1 | 0 | 1 | | | | | | | | |
| 1 | 1 | 0 | | | | | | | | |
| 1 | 1 | 1 | | | | | | | | |

Result

| | | |
|--------------------|-----|--|
| PREPARATION | 30 | |
| LAB PERFORMANCE | 30 | |
| REPORT | 40 | |
| TOTAL | 100 | |
| INITIAL OF FACULTY | | |

 PARITY GENERATOR/CHECKER:**Pin Diagram:****Truth Table:**

| INPUTS | | | OUTPUTS | |
|--------|-----|-------------------------------|---------------|--------------|
| EVEN | ODD | Σ of 1's at D0 THRU D7 | Σ EVEN | Σ ODD |
| 1 | 0 | EVEN | 1 | 0 |
| | | ODD | 0 | 1 |
| 0 | 1 | EVEN | 0 | 1 |
| | | ODD | 1 | 0 |
| 1 | 1 | X | 0 | 0 |
| 0 | 0 | X | 1 | 1 |

EVEN = 1, ODD = 0 \longrightarrow Parity checker

EVEN = 0, ODD = 1 \longrightarrow Parity generator

Output Table:

| CONTROL INPUT | | DATA BITS | | | | | | | | OUTPUTS | |
|---------------|-----|-----------|----|----|----|----|----|----|----|---------------|--------------|
| EVEN | ODD | D7 | D6 | D5 | D4 | D3 | D2 | D1 | D0 | Σ EVEN | Σ ODD |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | | |
| 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | | |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | | |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 0 | | |

Expt. No.: 5**Date:****DESIGN AND IMPLEMENTATION OF PARITY GENERATOR/
CHECKER****Aim**

To design and implement Parity Generator/Checker using Digital IC 74180.

Components Required

| S. No. | Description | Specification | Quantity |
|---------------|--------------------------|----------------------|-----------------|
| 1. | Parity Generator/Checker | IC 74180 | 1 |
| 2. | Digital Trainer Kit | - | 1 |
| 3. | Bread board | - | 1 |
| 4. | Power Supply | 5V | 1 |
| 5. | Connecting wires | - | As Required |


Procedure

- (i) Make the connections as per the logic diagram.
- (ii) Switch on the power supply.
- (iii) Apply various combinations of inputs according to the truth table and observe condition of output LEDs.
- (iv) Note down the outputs of Parity Generator/Checker for different combinations of input.

Result


| | | |
|---------------------------|------------|--|
| PREPARATION | 30 | |
| LAB PERFORMANCE | 30 | |
| REPORT | 40 | |
| TOTAL | 100 | |
| INITIAL OF FACULTY | | |

Pin Diagram:

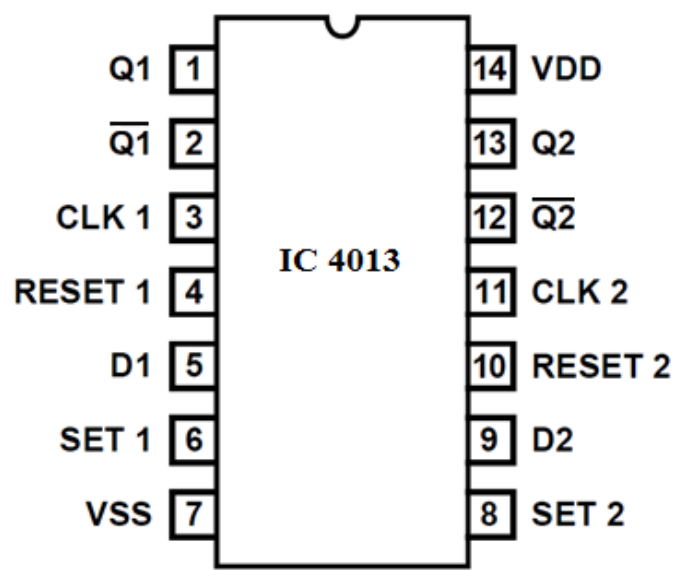

SERIAL IN SERIAL OUT SHIFT REGISTER:

Logic Diagram:

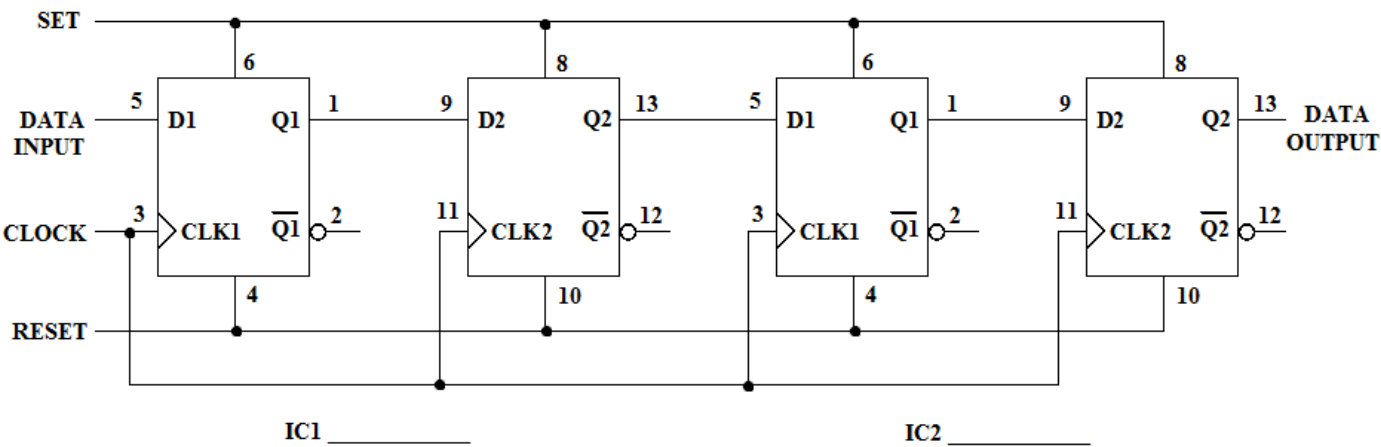

Output Table:

| CLK | DATA INPUT | DATA OUTPUT |
|-----|------------|-------------|
| 0 | 1 | |
| 1 | 0 | |
| 2 | 1 | |
| 3 | 0 | |
| 4 | 0 | |
| 5 | 1 | |

Expt. No.: 6**DESIGN AND IMPLEMENTATION OF SHIFT REGISTERS****Date:****Aim:**


To design and implement Shift Registers using Digital IC 4013.

Components Required:

| S. No. | Description | Specification | Quantity |
|--------|---------------------|---------------|-------------|
| 1. | D Flip Flop | IC 4013 | 2 |
| 2. | Digital Trainer Kit | - | 1 |
| 3. | Bread board | - | 1 |
| 4. | Power Supply | 5V | 1 |
| 5. | Connecting wires | - | As Required |

Procedure:


- (i) Make the connections as per the logic diagram.
- (ii) Switch on the power supply.
- (iii) Apply various combinations of inputs according to the truth table and observe condition of output LEDs.
- (iv) Observe the outputs of Shift Registers by providing consecutive clock pulses.

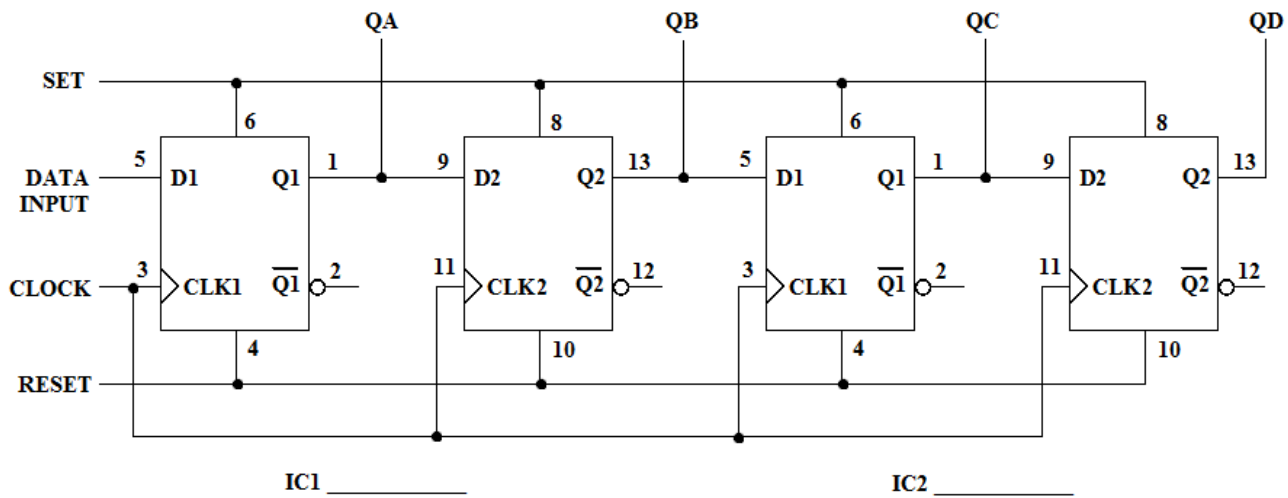SERIAL IN PARALLEL OUT SHIFT REGISTER:**Logic Diagram:**

DATA OUTPUTS : QA, QB, QC,QD

Output Table:

| CLK | DATA INPUT | DATA OUTPUTS | | | |
|-----|------------|--------------|----|----|----|
| | | QA | QB | QC | QD |
| 0 | 1 | | | | |
| 1 | 1 | | | | |
| 2 | 0 | | | | |
| 3 | 0 | | | | |
| 4 | 0 | | | | |

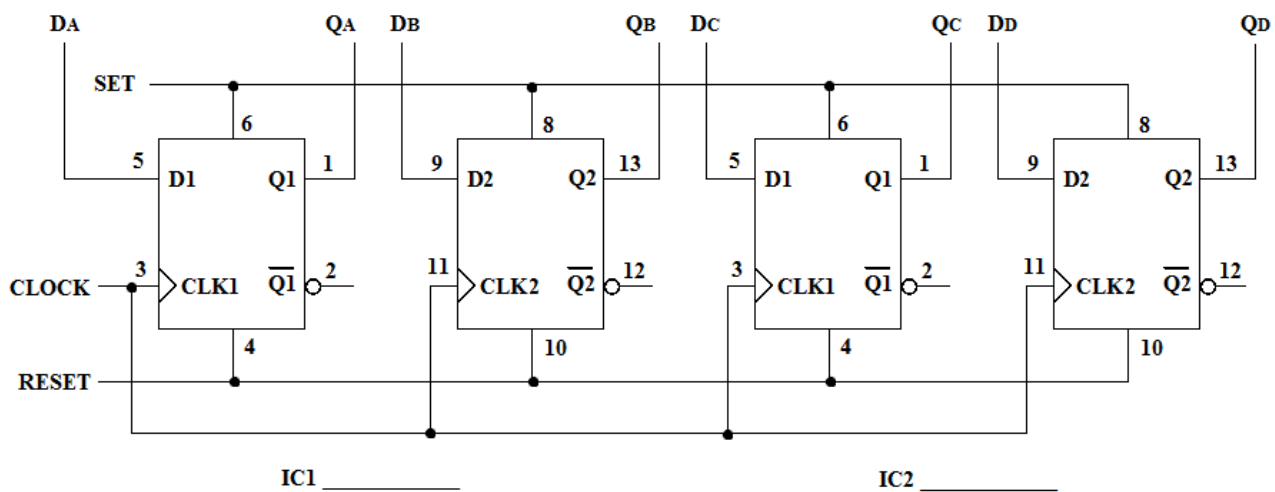PARALLEL IN PARALLEL OUT SHIFT REGISTER:**Logic Diagram:**

DATA INPUTS : DA, DB, DC,DD


DATA OUTPUTS : QA, QB, QC, QD

Output Table:

| CLK | DATA INPUTS | | | | DATA OUTPUTS | | | |
|-----|-------------|----|----|----|--------------|----|----|----|
| | DA | DB | DC | DD | QA | QB | QC | QD |
| 0 | 1 | 0 | 1 | 1 | | | | |
| 1 | 1 | 0 | 0 | 1 | | | | |
| 2 | 1 | 0 | 1 | 0 | | | | |
| 3 | 1 | 1 | 0 | 0 | | | | |
| 4 | 0 | 1 | 1 | 0 | | | | |

Result:

| | | |
|--------------------|-----|--|
| PREPARATION | 30 | |
| LAB PERFORMANCE | 30 | |
| REPORT | 40 | |
| TOTAL | 100 | |
| INITIAL OF FACULTY | | |

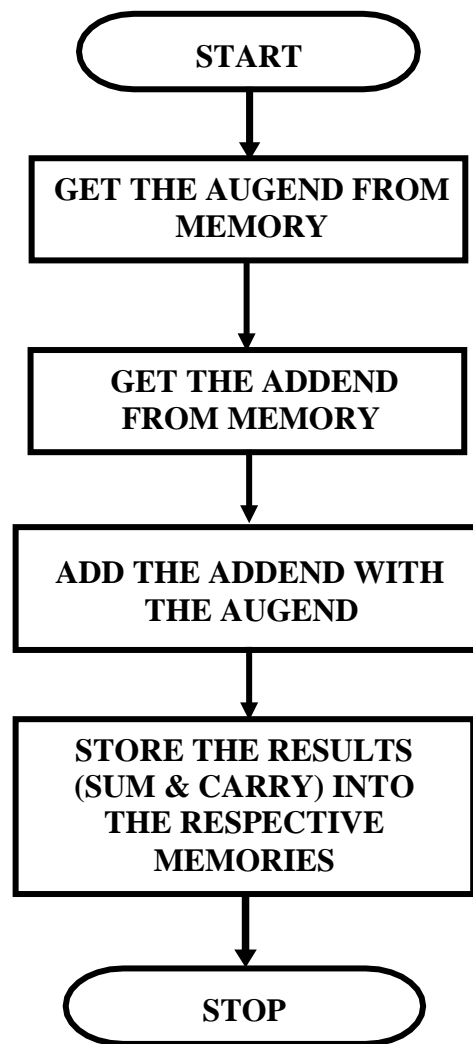FLOW CHART:

| | |
|---------------------|--|
| Expt. No.:7a | SIMPLE 8085 ASSEMBLY LANGUAGE PROGRAM: 8 BIT ARITHMETIC OPERATIONS (ADDITION) |
| Date: | |

Aim

To develop an 8085 Assembly Language Program (ALP) to test the addition of two 8-bit data available in the memory.

Problem Statement

1. Consider two 8-bit data X (Augend) and Y (Addend).
2. The Augend, X is in memory address 8500H and the Addend, Y is in memory address 8501H.
3. Find X+Y and store the results (Sum & Carry) in memory address 9000H and 9001H respectively.

Apparatus Required

| S. No | Apparatus name | Quantity |
|-------|--------------------------------|----------|
| 1 | 8085 microcomputer trainer kit | 1 |
| 2 | Power Supply (5V) | 1 |

Algorithm

Step1: Get the Augend from memory

Step2: Get the Addend from the next memory

Step3: Perform addition

Step4: Store the results of addition (Sum and Carry) to memory

Procedure

1. Connect +5V power supply to the 8085 microcomputer trainer kit.
2. Enter the opcode in the trainer kit using the matrix keyboard.
3. Check the opcode before execution of the program.
4. Enter the input data in the respective memories.
5. Execute the program.
6. Verify the result in the respective memories.

Assembly Language Program

| Address | Opcode | Label | Mnemonics | Comments |
|---------|--------|-------|-----------|----------|
| | | | | |


Input & Output Data:

| Input | |
|-------------------|------|
| Address | Data |
| 8500H (Augend) | |
| 8501H (Addend) | |

| Output | |
|------------------|------|
| Address | Data |
| 9000H (Sum) | |
| 9001H (Carry) | |

Result:

| | | |
|--------------------|-----|--|
| PREPARATION | 30 | |
| LAB PERFORMANCE | 30 | |
| REPORT | 40 | |
| TOTAL | 100 | |
| INITIAL OF FACULTY | | |

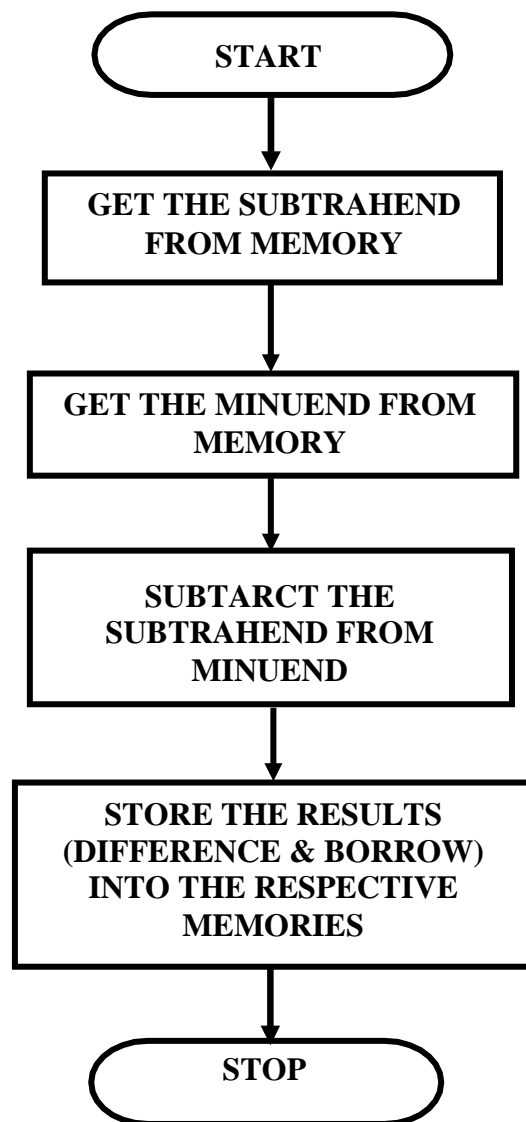FLOW CHART:

| | |
|---------------------|---|
| Expt. No.:7b | SIMPLE 8085 ASSEMBLY LANGUAGE PROGRAM: 8 BIT ARITHMETIC OPERATIONS (SUBTRACTION) |
| Date: | |

Aim

To develop an 8085 assembly language program (ALP) to test the subtraction of two 8-bit data available in the memory.

Problem Statement

1. Consider two 8 bit data X (Minuend) and Y (Subtrahend).
2. The Minuend, X is in memory address 8600H and Subtrahend, Y is in memory address 8601H.
3. Find X-Y and store the results (Difference & Borrow) in memory address 9000H and 9001H respectively.

Apparatus Required

| S. No | Apparatus Name | Quantity |
|--------------|--------------------------------|-----------------|
| 1 | 8085 microcomputer trainer kit | 1 |
| 2 | Power Supply (5V) | 1 |

Algorithm

Step1: Get the Subtrahend from memory

Step2: Get the Minuend from memory

Step3: Perform subtraction

Step4: Store the results of subtraction (Difference and Borrow) to memory

Procedure

1. Connect +5V power supply to the 8085 microcomputer trainer kit.
2. Enter the opcode in the trainer kit using the matrix keyboard.
3. Check the opcode before execution of the program.
4. Enter the input data in the respective memories.
5. Execute the program.
6. Verify the result in the respective memories.

Assembly Language Program

| Address | Opcode | Label | Mnemonics | Comments |
|---------|--------|-------|-----------|----------|
| | | | | |

Input & Output Data:

| Input | |
|-------------------------------|-------------|
| Address | Data |
| 8600H (Minuend) | |
| 8601H (Subtrahend) | |

| Output | |
|-------------------------------|-------------|
| Address | Data |
| 9000H (Difference) | |
| 9001H (Borrow) | |

Result

| | | |
|---------------------------|------------|--|
| PREPARATION | 30 | |
| LAB PERFORMANCE | 30 | |
| REPORT | 40 | |
| TOTAL | 100 | |
| INITIAL OF FACULTY | | |


 
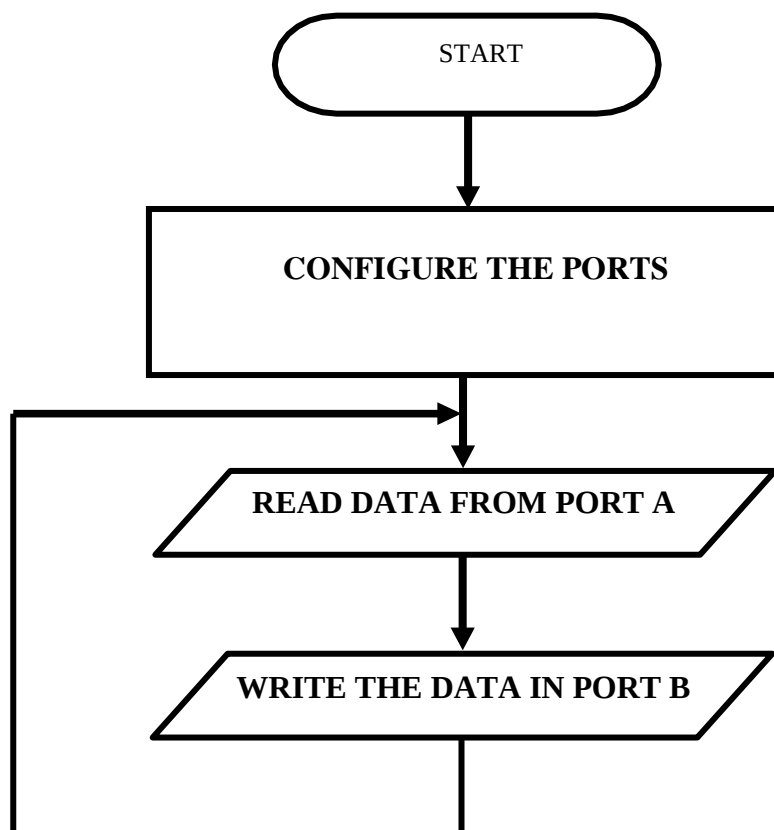


Fig 8.a: Block Diagram - 8255 with 8085 microprocessor

Flow Chart: (Mode 0)

 

Flow Chart: (BSR Mode)

Algorithm:**b. BSR mode:****Step1:** Configure Port C as an output port in mode 0**Step2:** Set Port C bits using BSR mode**Assembly language program:****b. BSR mode**

| ADDRESS | OPCODE | LABEL | MNEMONICS | COMMENTS |
|---------|--------|-------|-----------|----------|
| | | | | |

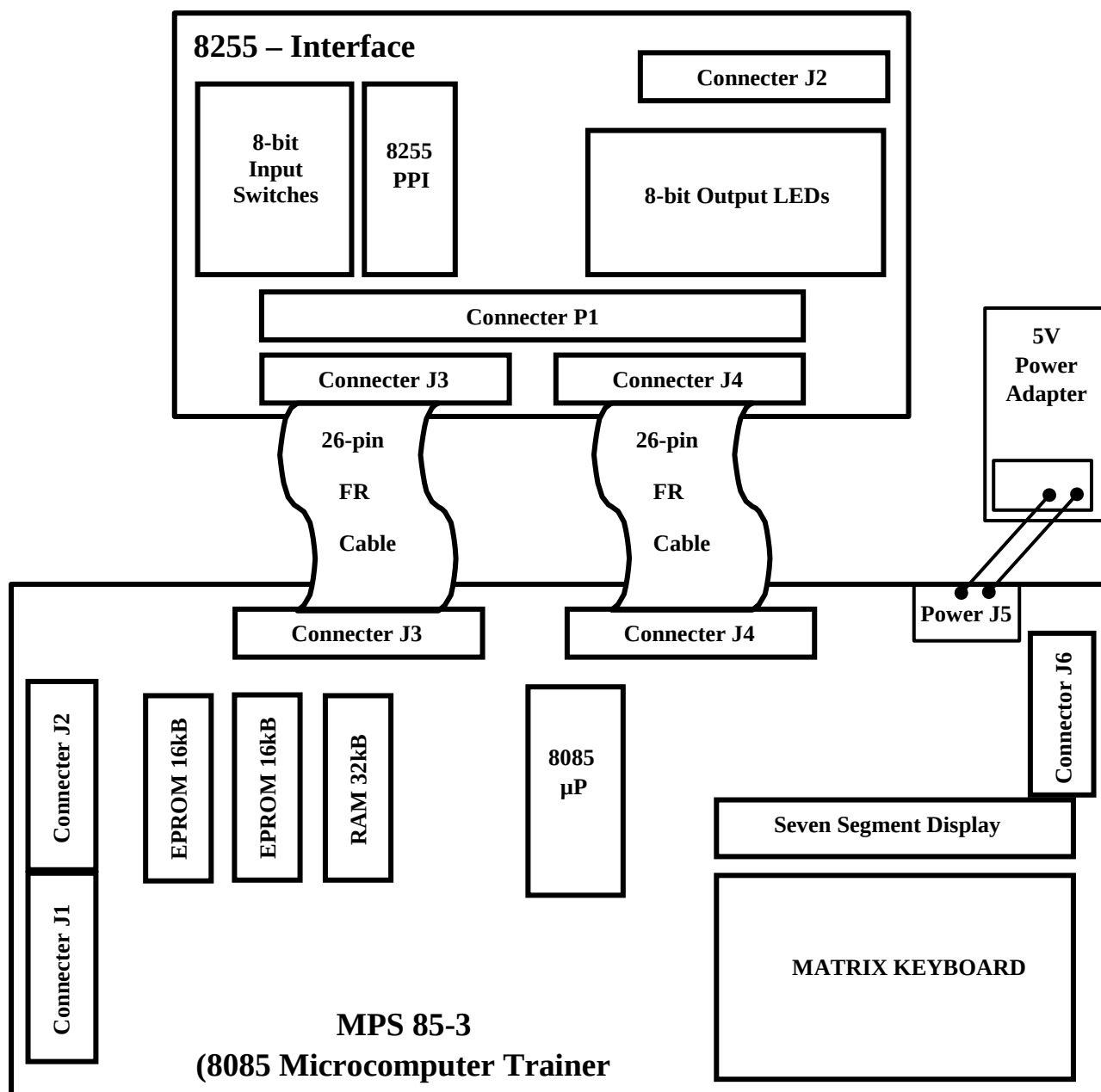


Fig 8.b: Interfacing diagram of 8255 with 8085 microprocessor

Procedure:**a. Mode 0:**

1. Connect +5V power supply to 8085 microcomputer trainer kit
2. Connect the 8255 - Interface Card with 8085 microcomputer trainer kit as shown in fig 5.b.
3. Manually configure the Port setting (Port A as input and Port B as output) in the 8255 – Interface Card using 8-way DIP switches.
4. Enter the opcode in the 8085 microcomputer trainer kit using matrix keyboard.
5. Check the opcode before execution of the program.
6. Execute the program.
7. Provide Input data to Port A using 8-way DIP switch connected to port A and Verify the output displayed in the LEDs connected to Port B.

b. BSR mode:

1. Connect +5V power supply to 8085 microcomputer trainer kit
2. Connect the 8255 - Interface Card with 8085 microcomputer trainer kit as shown in fig 5.b.
3. Enter the opcode in the 8085 microcomputer trainer kit using matrix keyboard.
4. Check the opcode before execution of the program.
5. Execute the program.
6. Verify the output displayed in the LEDs connected to Port C.



Output**a. For mode 0 Before execution:**

| PA7 | PA6 | PA5 | PA4 | PA3 | PA2 | PA1 | PA0 |
|-----|-----|-----|-----|-----|-----|-----|-----|
| | | | | | | | |

| PB7 | PB6 | PB5 | PB4 | PB3 | PB2 | PB1 | PB0 |
|-----|-----|-----|-----|-----|-----|-----|-----|
| | | | | | | | |

After execution:

| PA7 | PA6 | PA5 | PA4 | PA3 | PA2 | PA1 | PA0 |
|-----|-----|-----|-----|-----|-----|-----|-----|
| | | | | | | | |

| PB7 | PB6 | PB5 | PB4 | PB3 | PB2 | PB1 | PB0 |
|-----|-----|-----|-----|-----|-----|-----|-----|
| | | | | | | | |

b. For BSR Mode**Before execution:**

| PC7 | PC6 | PC5 | PC4 | PC3 | PC2 | PC1 | PC0 |
|-----|-----|-----|-----|-----|-----|-----|-----|
| | | | | | | | |

After execution:

| PC7 | PC6 | PC5 | PC4 | PC3 | PC2 | PC1 |
|-----|-----|-----|-----|-----|-----|-----|
| | | | | | | |

Note: Fill “0” to indicate OFF state of LED and “1” to indicate ON state of LED in 8255 - Interface card.

RESULT

| | | |
|---------------------------|------------|--|
| PREPARATION | 30 | |
| LAB PERFORMANCE | 30 | |
| REPORT | 40 | |
| TOTAL | 100 | |
| INITIAL OF FACULTY | | |

 


Fig 9.a: Block Diagram - Stepper motor with 8085 microprocessor through 8255

*The stepper motor coils are connected to the Port bits as shown in the table below

| Coil | Port Bit |
|------|----------|
| A | PA3 |
| B | PA2 |
| C | PA1 |
| D | PA0 |

Expt. No.: 9

INTERFACING OF STEPPER MOTOR WITH 8085 MICROPROCESSOR

Date:

Aim

To develop an 8085 ALP to interface the stepper motor with 8085 microprocessor and to rotate the stepper motor in the following sequences:

- a. Full step sequence b. Half step sequence

Problem statement

- a. Full step sequence:
Rotate the stepper motor in the clockwise direction in full step sequence.
- b. Half step sequence:
Rotate the stepper motor in the clockwise direction in half step sequence.

Apparatus required


| S. No | Apparatus Name | Quantity |
|-------|--|----------|
| 1 | 8085 microprocessor trainer kit | 1 |
| 2 | Power Supply (+5V) | 1 |
| 3 | 4 Phase Uni-polar Stepper Motor | 1 |
| 4 | Stepper Motor driver kit | 1 |
| 5 | 26 pin FRC Cable | 1 |
| 6 | +5V Power Adapter for Stepper motor driver kit | 1 |

Algorithm:**a. Full step sequence**

- Step1:** Initialize Port A of 8255 as an output port
Step2: Write the bit pattern to port A to energize a coil
Step3: Call delay routine
Step4: Rotate the bit pattern to energize the successive coil
Step5: Go to step 2

Algorithm:**b. Half step sequence**

- Step1:** Initialize Port A of 8255 as an output port
Step2: Initialize the size (count) of the lookup table in a register
Step3: Point the starting address of the lookup table which has the bit pattern of half step sequence
Step4: Write the bit patterns available in the successive memory of lookup table to Port A with a delay
Step5: After writing all the bit pattern in the lookup table, go to step2

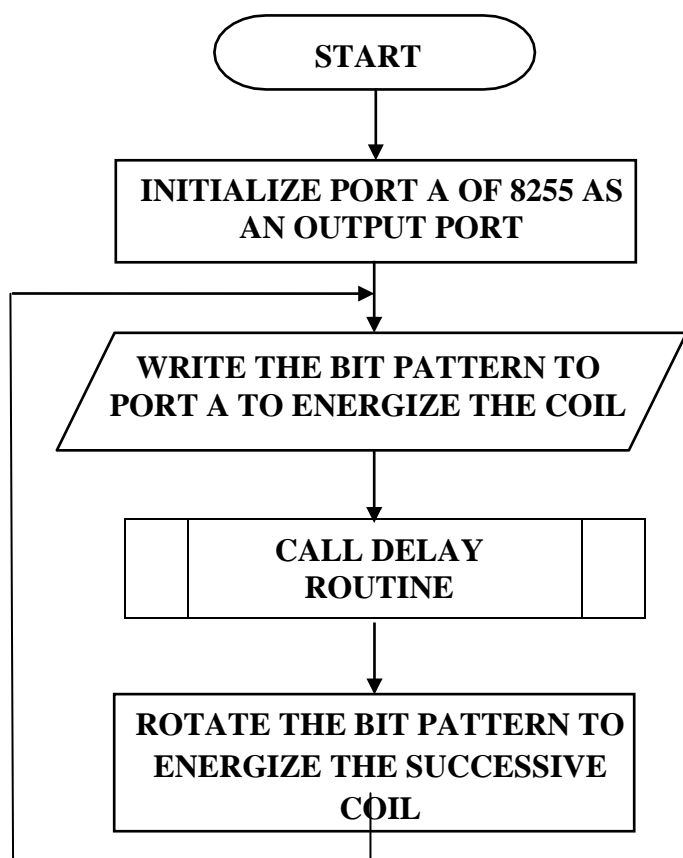FLOWCHART:**FULL STEP IN CLOCKWISE DIRECTION****FULL STEP SEQUENCE PATTERN:**

| STEPS | COILS | | | |
|-------|-------|---|---|---|
| | A | B | C | D |
| 1 | 1 | 0 | 0 | 0 |
| 2 | 0 | 1 | 0 | 0 |
| 3 | 0 | 0 | 1 | 0 |
| 4 | 0 | 0 | 0 | 1 |

| D7 | D6 | D5 | D4 | D3 | D2 | D1 | D0 |
|----|----|----|----|-----|-----|-----|-----|
| - | - | - | - | PA3 | PA2 | PA1 | PA0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 |

| HEX DATA |
|----------|
| 88H |
| 44H |
| 22H |
| 11H |

[OR]

| STEPS | COILS | | | |
|-------|-------|---|---|---|
| | A | B | C | D |
| 1 | 1 | 1 | 0 | 0 |
| 2 | 0 | 1 | 1 | 0 |
| 3 | 0 | 0 | 1 | 1 |
| 4 | 1 | 0 | 0 | 1 |

| D7 | D6 | D5 | D4 | D3 | D2 | D1 | D0 |
|----|----|----|----|-----|-----|-----|-----|
| - | - | - | - | PA3 | PA2 | PA1 | PA0 |
| 1 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 | 0 |
| 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 |


| HEX DATA |
|----------|
| CCH |
| 66H |
| 33H |
| 99H |

a. Full step sequence

| ADDRESS | OPCODE | LABEL | MNEMONICS | COMMENTS |
|---------|--------|-------|-----------|----------|
| | | | | |


FLOWCHART: (HALF STEP IN CLOCKWISE DIRECTION)**HALF STEP SEQUENCE PATTREN:**

| STEP | A | B | C | D | HEX CODE |
|------|---|---|---|---|----------|
| 1 | 1 | 0 | 0 | 0 | 08H |
| 2 | 1 | 1 | 0 | 0 | 0CH |
| 3 | 0 | 1 | 0 | 0 | 04H |
| 4 | 0 | 1 | 1 | 0 | 06H |
| 5 | 0 | 0 | 1 | 0 | 02H |
| 6 | 0 | 0 | 1 | 1 | 03H |
| 7 | 0 | 0 | 0 | 1 | 01H |
| 8 | 1 | 0 | 0 | 1 | 09H |

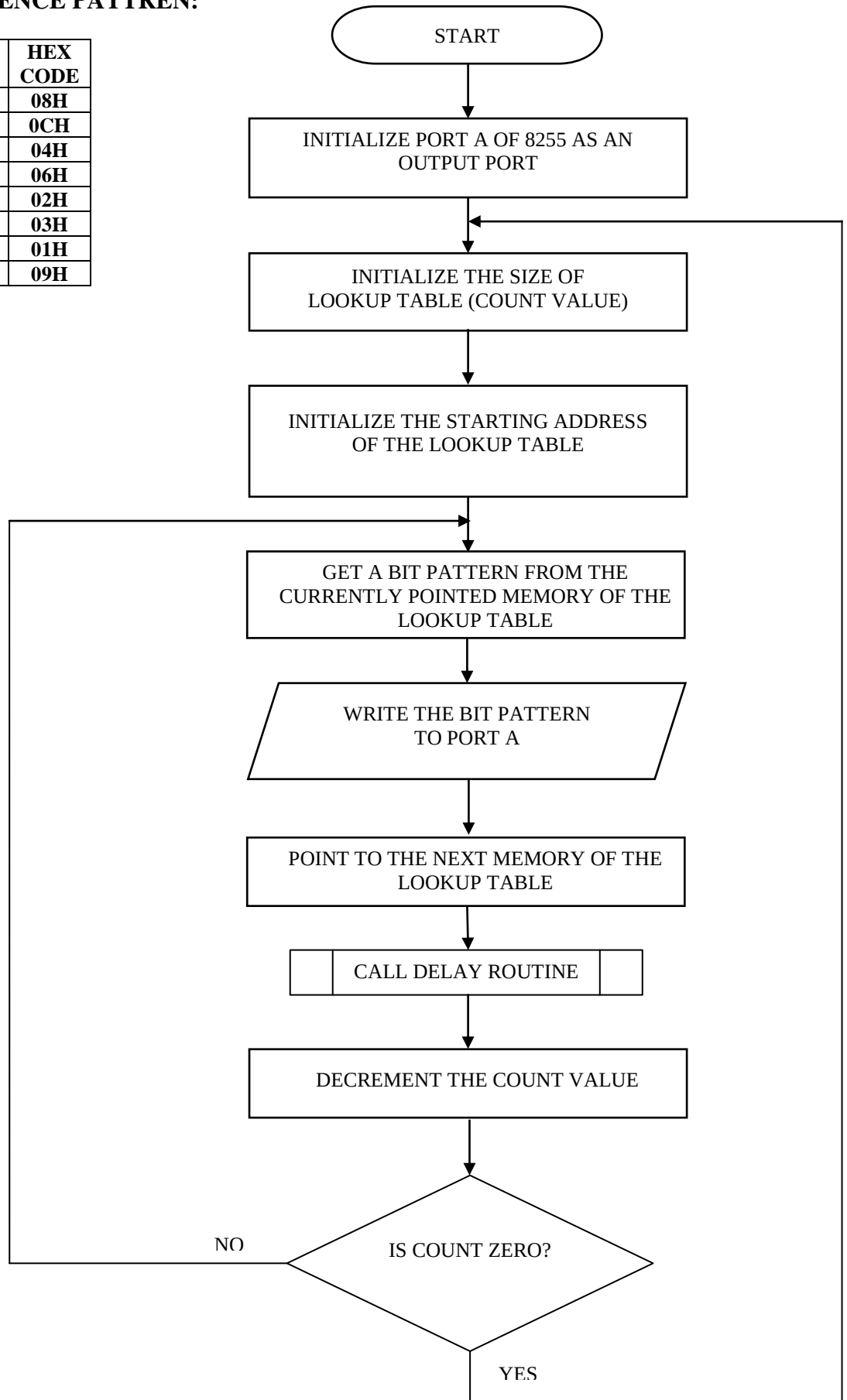

b. Half step sequence

| ADDRESS | OPCODE | LABEL | MNEMONICS | COMMENTS |
|---------|--------|-------|-----------|----------|
| | | | | |

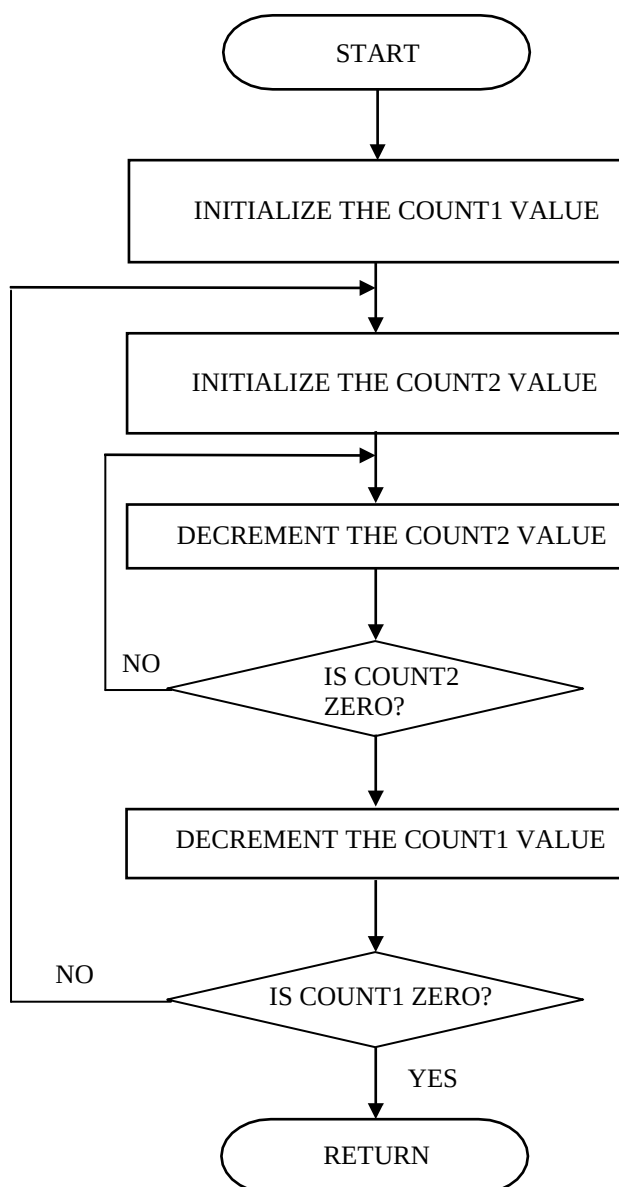FLOWCHART: DELAY ROUTINE

Lookup table for half step sequence in Clockwise direction:

| MEMORY LOCATIONS | DATA |
|------------------|------|
| | 08H |
| | 0CH |
| | 04H |
| | 06H |
| | 02H |
| | 03H |
| | 01H |
| | 09H |

| ADDRESS | OPCODE | LABEL | MNEMONICS | COMMENTS |
|---------|--------|-------|-----------|----------|
| | | | | |


Procedure:


1. Connect +5V power supply to 8085 microcomputer trainer kit
2. Interface the Stepper motor with the driver board and interface the driver board with 8085 microprocessor through 8255 as shown in fig 9.b or 9.c
3. Enter the opcode in the 8085 microcomputer trainer kit using matrix keyboard
4. Check the opcode before execution of the program
5. Execute the program
6. Verify that the stepper motor starts rotating

RESULT

| | | |
|---------------------------|------------|--|
| PREPARATION | 30 | |
| LAB PERFORMANCE | 30 | |
| REPORT | 40 | |
| TOTAL | 100 | |
| INITIAL OF FACULTY | | |

PIN ASSIGNMENT WITH 8085
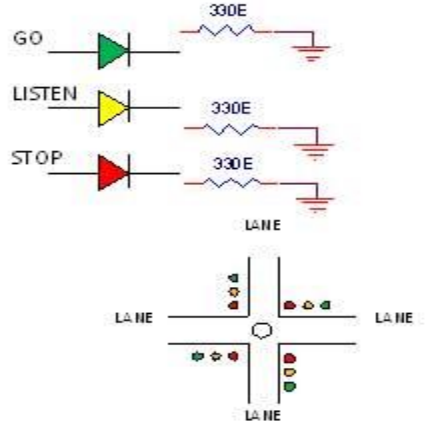
| LAN Direction | 8255 PORT PINS | LEDs | Traffic Light Controller Card |
|---------------|----------------|------------|---|
| SOUTH | | GREEN |  <p>Make high to - LED On Make low to - LED Off</p> |
| | | YELLOW | |
| | | RED | |
| | | PEDESTRIAN | |
| EAST | | GREEN | |
| | | YELLOW | |
| | | RED | |
| | | PEDESTRIAN | |
| NORTH | | GREEN | |
| | | YELLOW | |
| | | RED | |
| | | PEDESTRIAN | |
| WEST | | GREEN | |
| | | YELLOW | |
| | | RED | |
| | | PEDESTRIAN | |
| PWR | | VCC | Supply form 8085 Microcomputer Trainer Kit at connector J2 |
| | | GND | |

 CIRCUIT DIAGRAM TO INTERFACE TRAFFIC LIGHT WITH 8085**Fig 10: Interfacing of stepper motor with 8085 microprocessor using 8255**

Expt. No.:10

INTERFACING OF TRAFFIC LIGHT CONTROLLER WITH 8085 MICROPROCESSOR

Date:

Aim

To develop an 8085 ALP to interface traffic light controller and to generate a sequence of lighting to control the traffic.

Problem statement

Control the 4 lane Traffic light signal interfaced with 8085 microprocessor through 8255 by generating a proper sequence of lighting.

Apparatus required

| S. No | Apparatus Name | Quantity |
|-------|---------------------------------|----------|
| 1 | 8085 microprocessor trainer kit | 1 |
| 2 | Traffic light controller module | 1 |
| 3 | +5V DC Power Adapter | 1 |

Algorithm:

Step1: Initialize all ports of 8255 as output port

Step2: Write the bit pattern to generate the lighting sequence to control the traffic

Step3: Call delay routine

Step4: Go to step 2

Procedure:

1. Connect +5V power supply to 8085 microcomputer trainer kit
2. Interface the traffic light controller with 8085 microprocessor through 8255 as shown in fig 10
3. Enter the opcode in the 8085 microcomputer trainer kit using matrix keyboard
4. Check the opcode before execution of the program
5. Execute the program
6. Verify that the sequence of lighting generated to control the traffic

| ADDRESS | OPCODE | LABEL | MNEMONICS | COMMENTS |
|---------|--------|-------|-----------|----------|
| | | | | |

| ADDRESS | OPCODE | LABEL | MNEMONICS | COMMENTS |
|---------|--------|-------|-----------|----------|
| | | | | |

RESULT

| | | |
|---------------------------|------------|--|
| PREPARATION | 30 | |
| LAB PERFORMANCE | 30 | |
| REPORT | 40 | |
| TOTAL | 100 | |
| INITIAL OF FACULTY | | |

